

Chapter #4

Electric current & circuits



We will discuss:-

- Electric charges.
- The flow of charges.
- How charges interact.
- Electricity , circuit, current ,electricity, repulsion and attraction.
- Capacitance.
- Medical use of capacitors.
- Potential difference (voltage)
- Power
- Conventional current direction.
- Resistance.
- Ohm's law.
- Series and parallel circuits.
- Capacitors in series and parallel.

Electric charges.


- The atom is made up of three main parts:-

Protons, neutrons and electrons.

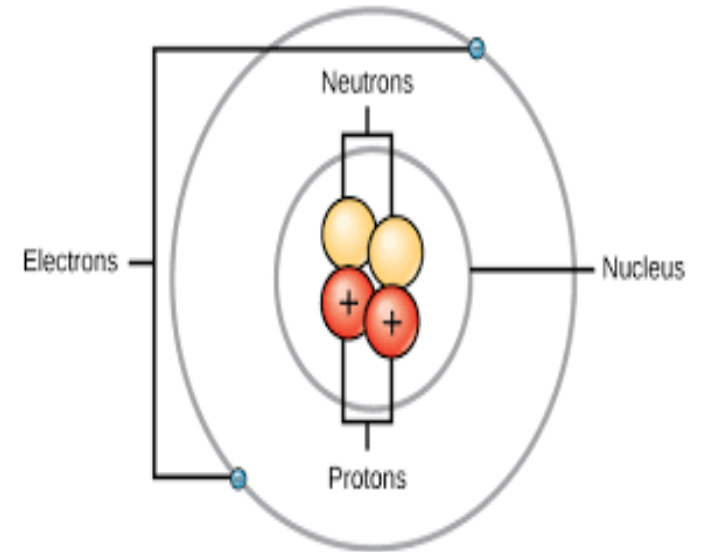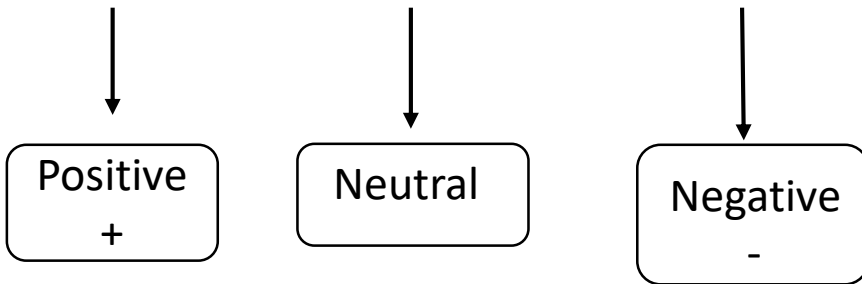


The flow of charges.

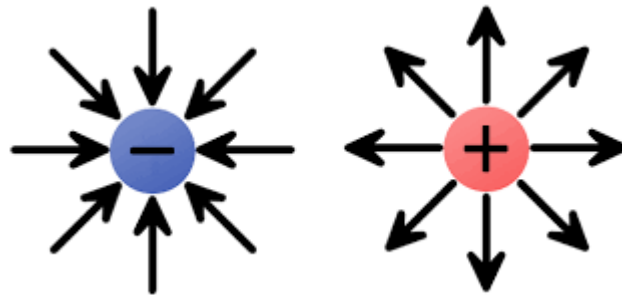- **Electrons** :The subatomic particle which can move from one object to another.
- The object will be **Negatively** charged when we **add** electrons to the object.
- The object will be **positively** charged when we **remove** electrons from the object.





How charges interact?

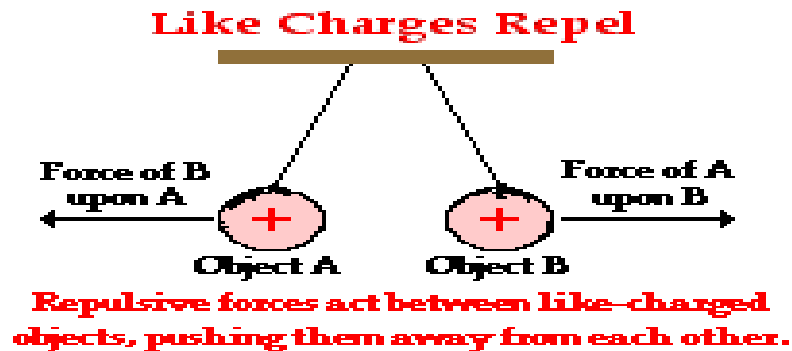- When two objects with same charge come into contact they will repel.



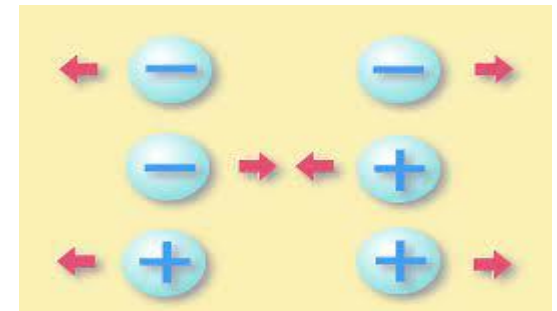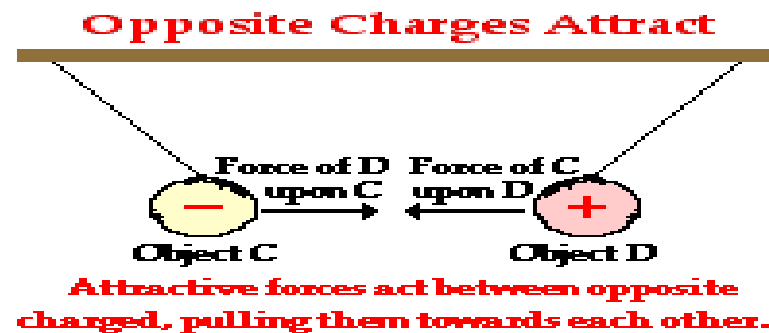- When two objects with different charges come into contact they will attract.



How charges interact?

Coulomb's Law – Gives the electric force between two point charges.


$$F = k \frac{q_1 q_2}{r^2} \quad \text{Inverse Square Law}$$

k = Coulomb's Constant = $9.0 \times 10^9 \text{ Nm}^2/\text{C}^2$

q_1 = Point charge - 1

q_2 = Point charge - 2

r = the distance between the two charges

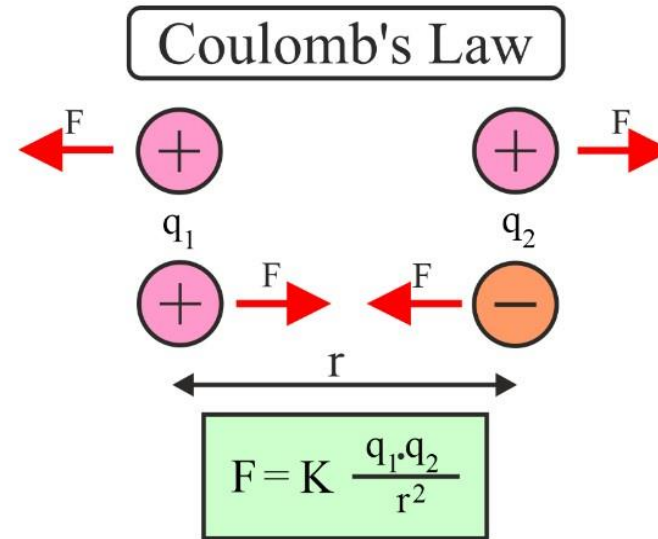


Definition.

- **Electricity** : a form of energy .
- **Circuit**: a continuous path through which electrons can flow.
- **Current electricity**: the study of charge that move
- **Repulsion** :is the movement away from each other.
- **Attraction**: is the movement towards each other.
- **Static electricity** : is the study of charges that do not move.

Capacitance.


- Capacitor: electric device for storing charge.
- The symbol of charge (Q), it measured in units called coulombs (C).
- The charge can be positive or negative .

What is capacitor?

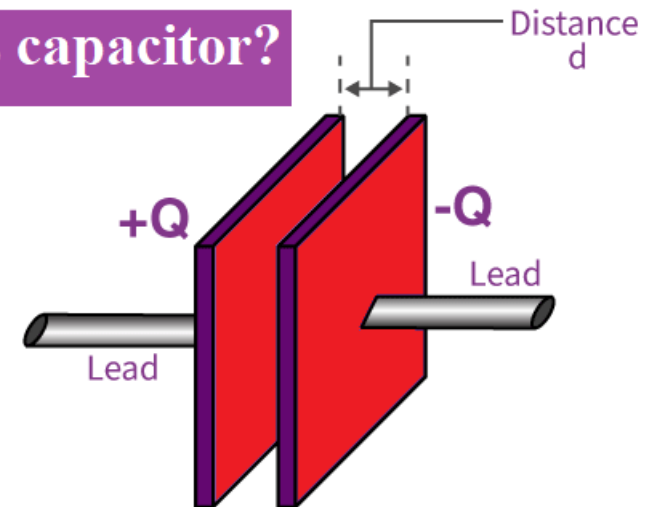

Parallel Plate Capacitor

Capacitance.

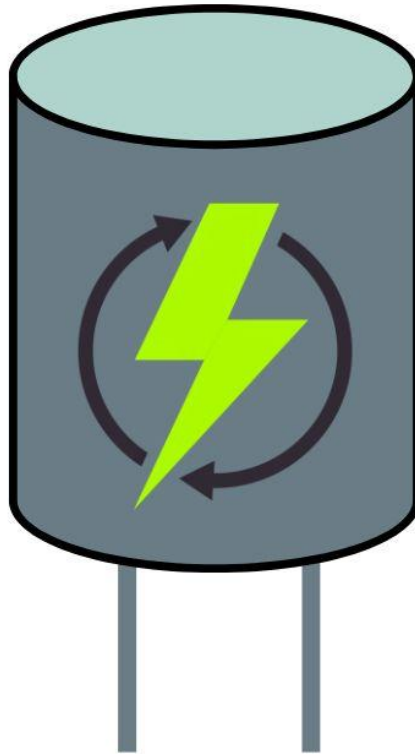

CAPACITANCE

CAPACITANCE IS A FUNDAMENTAL ELECTRICAL PROPERTY THAT MEASURES THE ABILITY OF A CAPACITOR TO **STORE ELECTRICAL CHARGE**. IT IS DENOTED BY THE SYMBOL "C" AND IS MEASURED IN UNITS CALLED FARADS (F).


The medical use of capacitors

- A **defibrillator** machine is a medical device that uses a single very large capacitor
- This machine gives a patient an electric shock across his heart.
- The shock stops the heart beating erratically (fibrillation)




What is fibrillation?

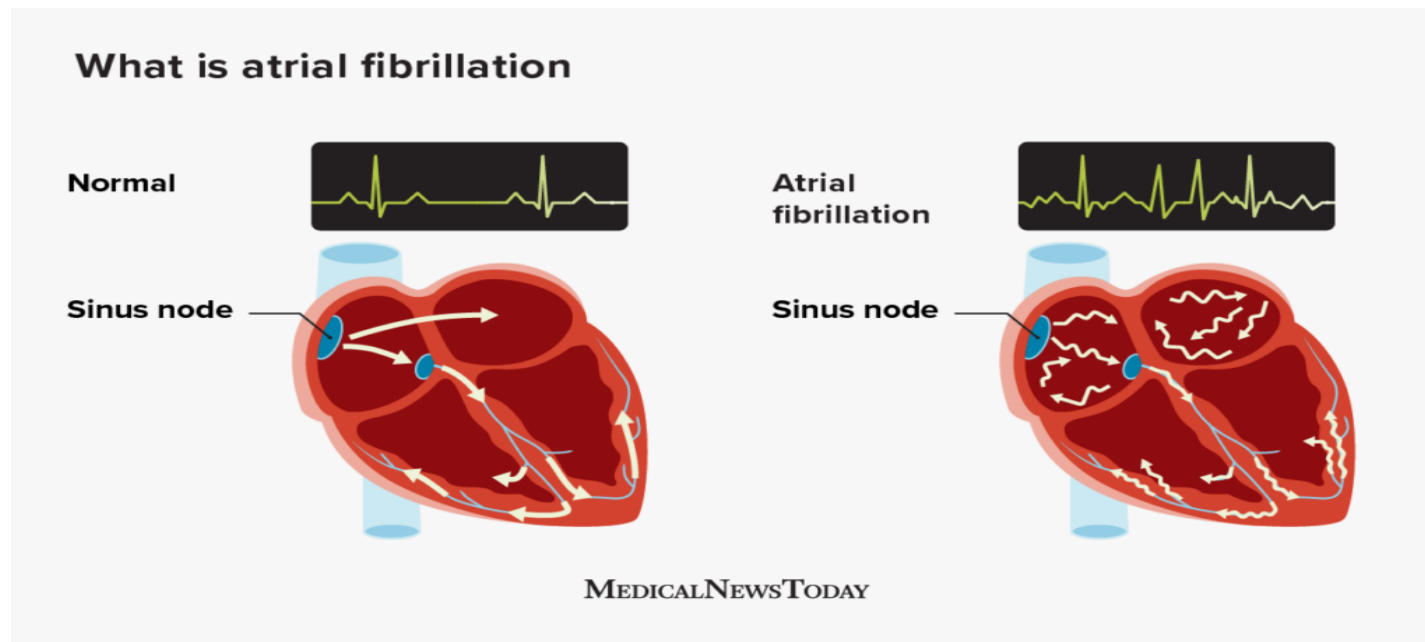- **Atrial fibrillation** (also called AFib or AF) is an irregular heartbeat (arrhythmia) that can lead to blood clots, stroke, heart failure and other heart-related complications.




What is fibrillation?

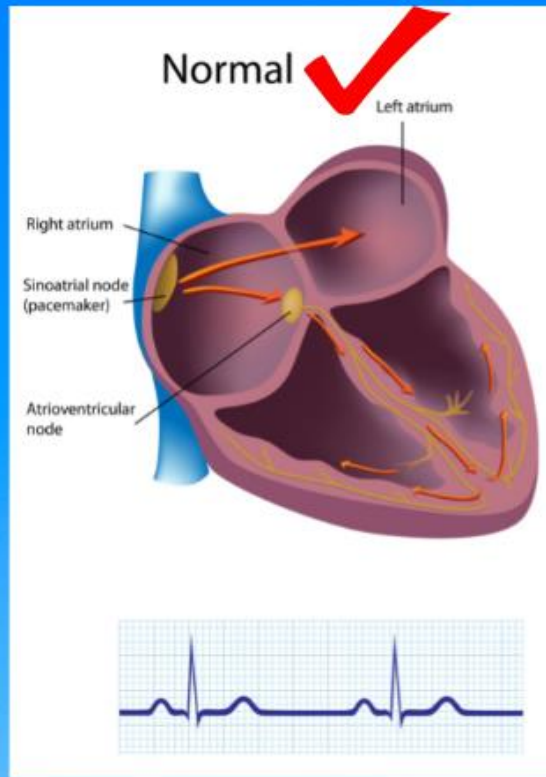

What Is AFib?

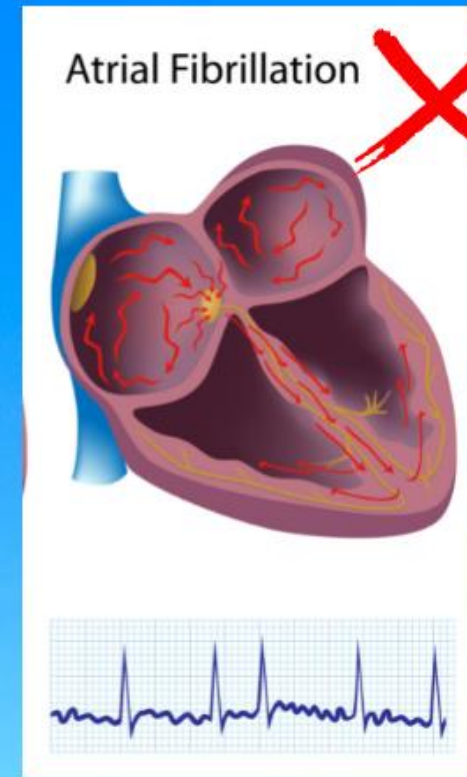In atrial fibrillation, the normal, steady electrical activity of the heartbeat is replaced by the rapid, irregular electrical signals of AFib.



Defibrillation

- **Defibrillation**: is the process in which an electronic device sends an electric shock to the heart to stop an extremely rapid, irregular heartbeat and restore the normal heart rhythm.
- **Defibrillators** can also restore the heart's beating if the heart suddenly stops.
- **Defibrillators** help to stop **fibrillation**.



Electric current .

- Electric current : is a flow of charged particles.
- Symbol : I
- The SI unit of electric current is ampere (A)
- Formula : $I = \frac{q}{t} = \text{Coulomb} / \text{sec} = \text{C/s} = 1 \text{ amp}$
- Where q is the charge , t is the time

A flow of electric charge, it is measured in amperes (A)



Example 1


- if a current of 80mA exists in a metal wire , how many electrons flow past a given cross-section of the wire in 10 minutes ?

Potential difference (Voltage)

- When a point charge q moves from point A to point B, it moves through a potential difference
- **The potential difference** is the change in electric potential energy per unit charge.
- **Voltage** describes the “pressure” that pushes electricity. The amount of voltage is indicated by a unit known as the **volt (V)**, and higher voltages cause more electricity to flow to an electronic device. However, electronic devices are designed to operate at specific voltages; excessive voltage can damage their circuitry.

Potential difference (Voltage)

- Electricity flows as a current. You can imagine it as a flow of water, like in a river. The water in rivers flows from mountains upstream to the ocean downstream. In other words, water flows from places with a high water height to places with a low water height. Electricity acts similarly: the concept of water height is analogous to electric potential, and electricity flows from places with high electric potential to places with low electric potential.

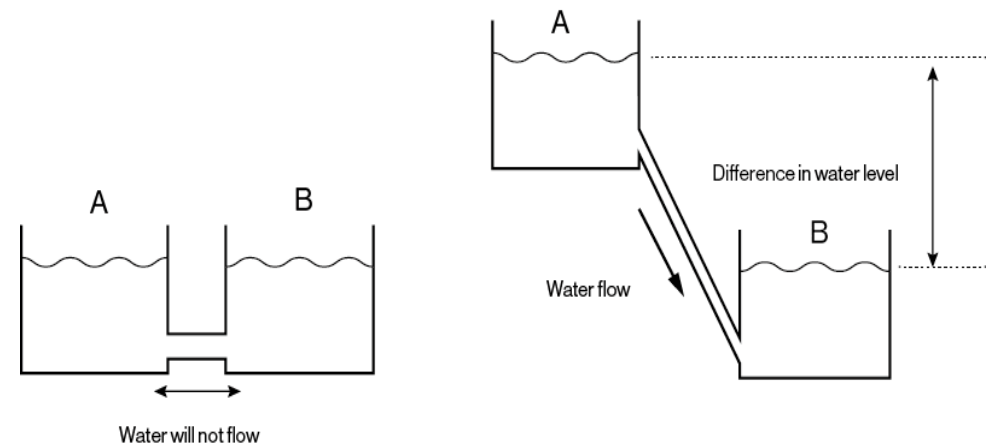

Potential difference (Voltage)


- **Formula** : $V = \frac{W}{Q}$ =joules/coulomb =volts

- Batteries

- Outlets

- **EKG** : records the electrical signal from the heart to check for different heart conditions

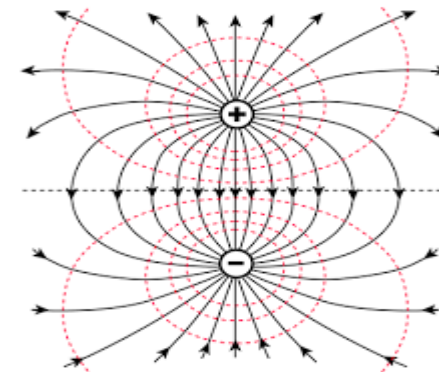- Equipotential lines: points at same potential.




Part of circuits

- **Energy Source** :circuit needs an energy source to push a charge through the circuit.
- **Load** : a device in a circuit that operates using electrical energy.

Electric Circuits


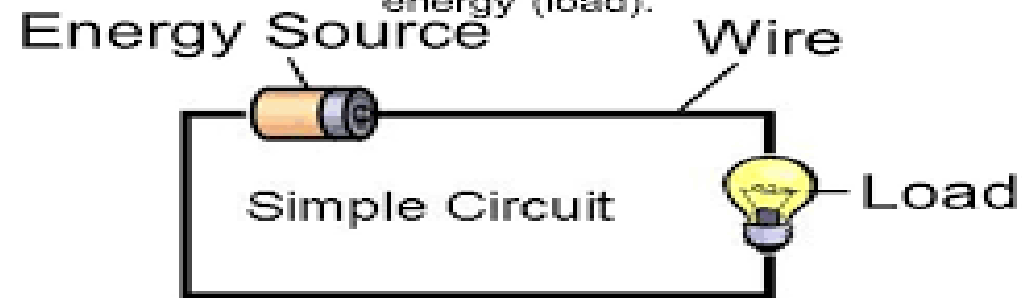
All circuits need three basic parts: an energy source, wires, and the object that is going to change the electrical energy into another form of energy (load).



Power

- Power : Electric power is the rate at which electrical energy is transferred by an electric circuit.
- Symbol: P
- Formula : $P = \frac{W}{t} = \frac{\text{joule}}{\text{Second}} = \text{watt (W)}$
- $P = IV$
- The SI unit of the power is **watt**

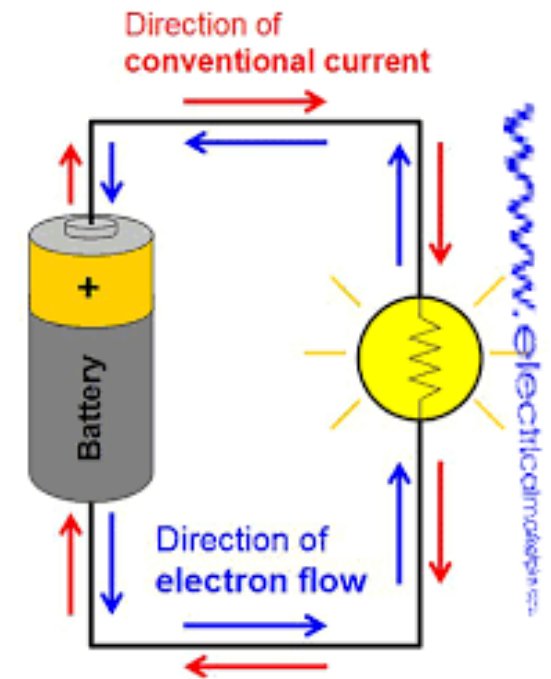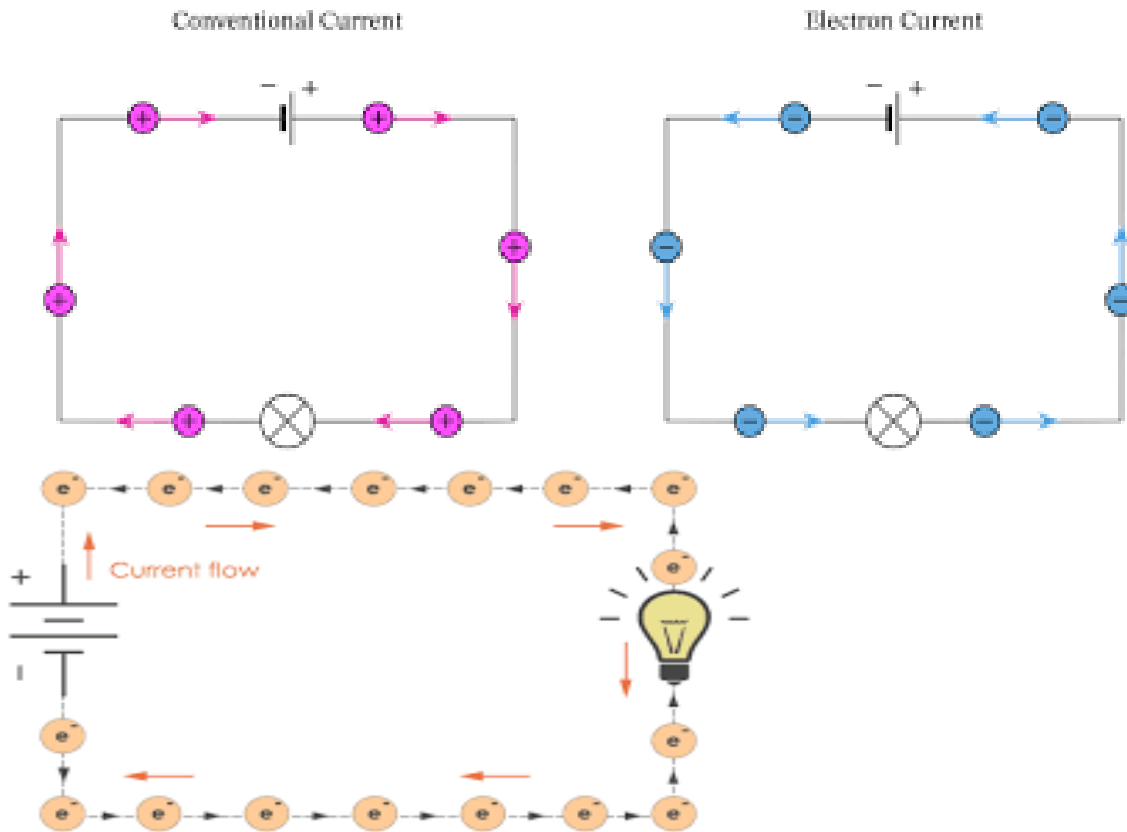Conventional current direction and electrons flow direction



Electrical resistance




- **Resistance** is a measure of the opposition to current flow in an electrical circuit.
- Resistance is measured in **ohms Ω** .
- The symbol of resistance (R) .



- Long wire has a higher resistance.
- The ratio of voltage to current is called **resistance**





$$R = \frac{V}{I}$$

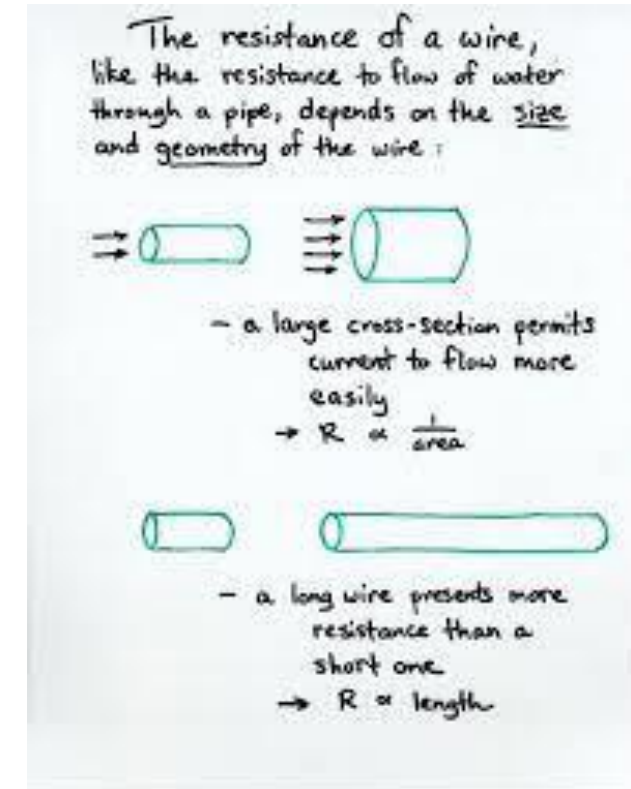

Ohm's law

- **ohm's law** : a law stating that electric current is proportional to voltage and inversely proportional to resistance.


- $V = IR$

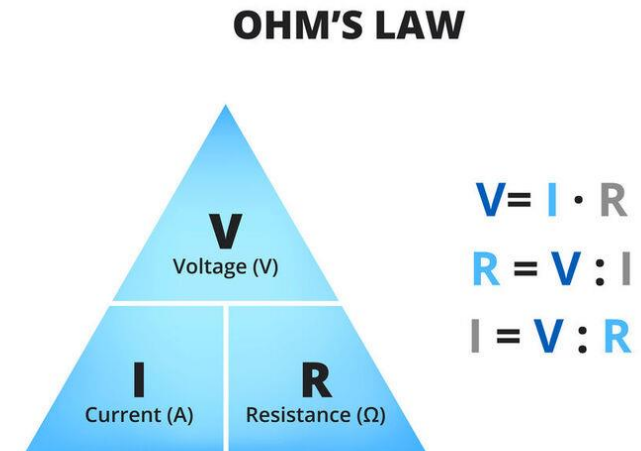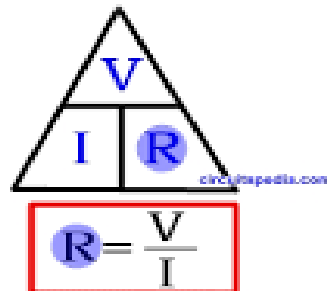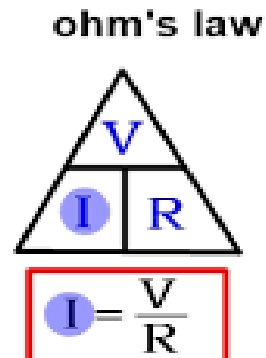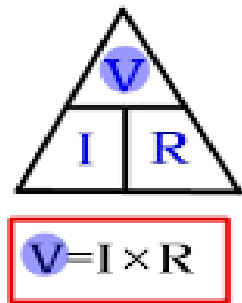




Ohm`s law

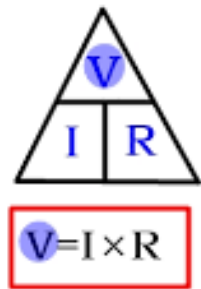- Example 2:

calculate the current if the voltage $v=24$ volts and $R=8\Omega$?




ohm's law

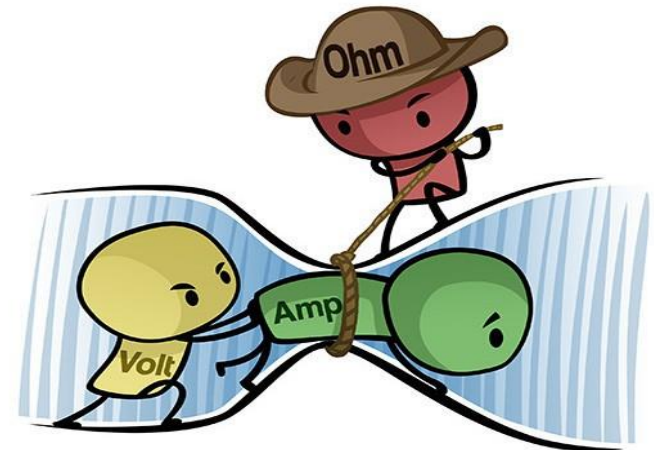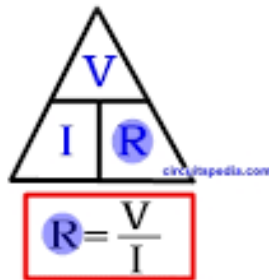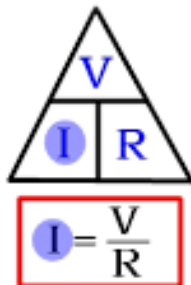

electric circuits

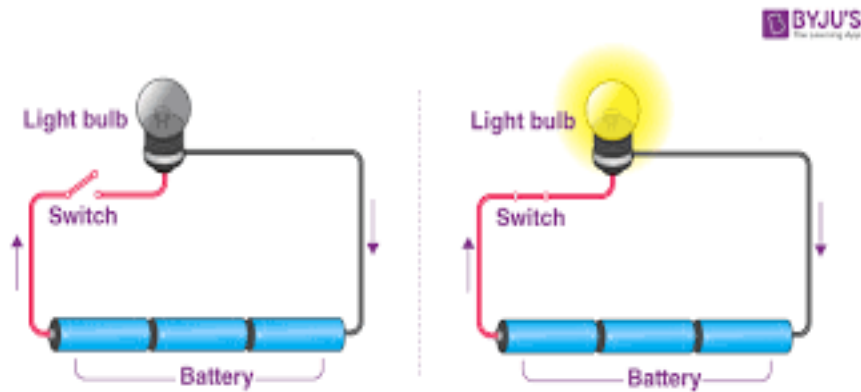- Electric circuits: path for transmitting electric current .




- We will study two types of electric circuits , **Series and parallel** circuits.

Series Circuits

- A series circuit is defined as the circuit in which a number of resistances are connected one after the other.
- In a series circuit, the flow of current follows a single path.

Series Circuit:

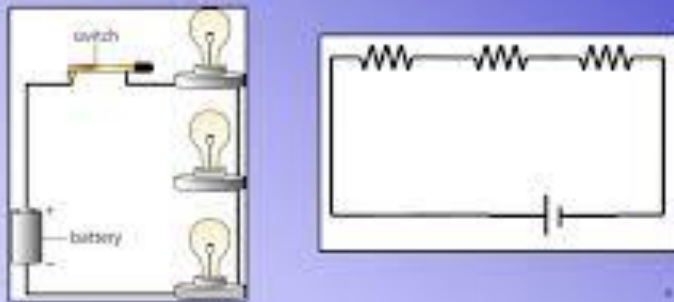
Circuit in which a current flows through each component, one after another. There is only one path for the current to follow.



Series Circuits

- What is the formula for resistance in series ?

$$R_{eq} = R_1 + R_2 + R_3$$

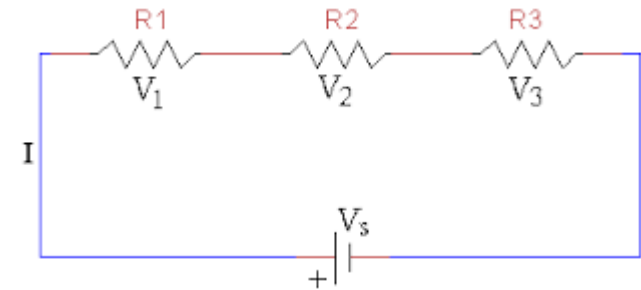


- **The current in a series circuit** goes through every component in the circuit. Therefore, all of the components in a series connection carry the **same current**. A series circuit has only one path through which its current can flow.
- The voltages In a series circuit, **the sum of the voltages across** components is equal to the supply voltage.

Series Circuits

- **Example 3 :**

In the circuit shown in the figure, two resistors R_1 and R_2 have been connected in series


Find : R_{eq} , I , V_1 , V_2 , ?

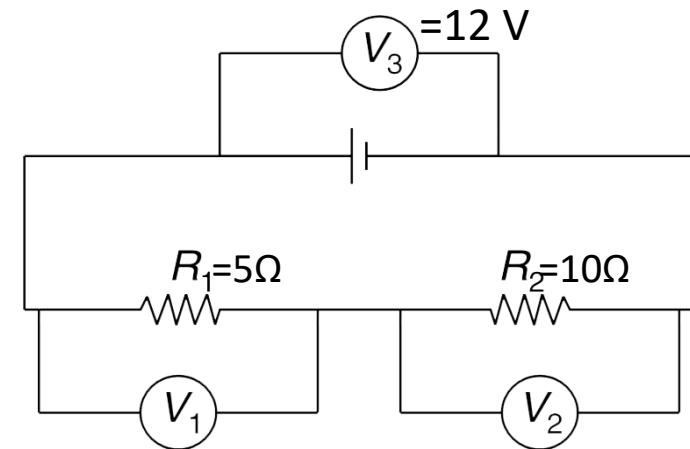

Series Circuits

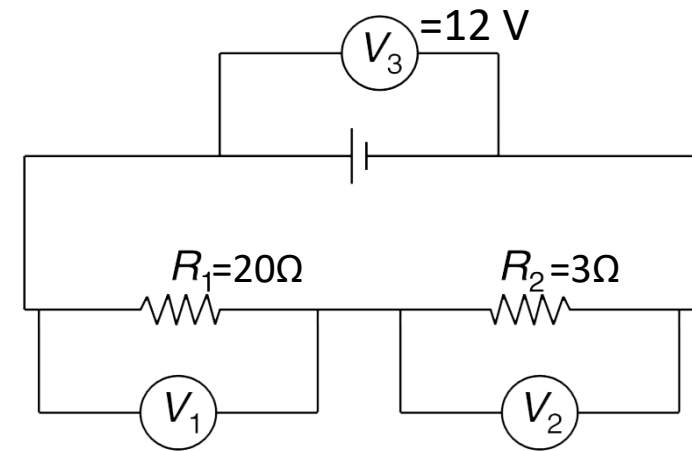
- **Example 4 :**

In the circuit shown in the figure, which resistor will take more voltage



Parallel circuits

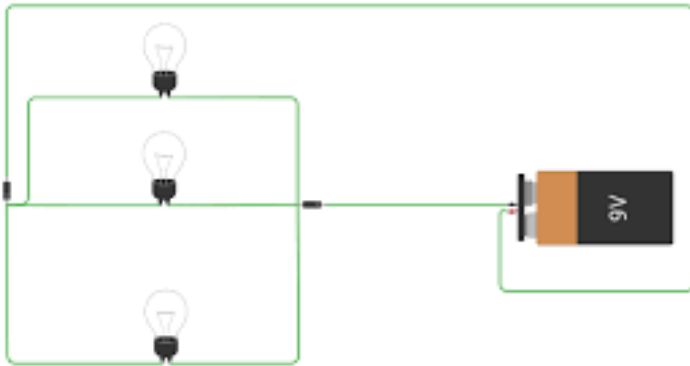
- Parallel circuit, an electrical path that branches so that the current divides and only part of it flows through any branch.



Parallel circuits

- What is the formula for the resistance in parallel ?
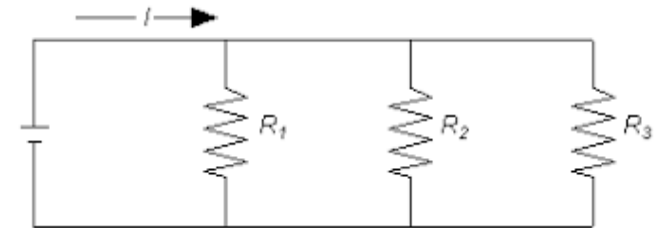
$$R_{eq} = \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right)^{-1}$$




- The current in a parallel circuit **splits** into different branches then combines again before it goes back into the supply.
- Voltage is the **same** across each component of the parallel circuit.

Parallel circuits

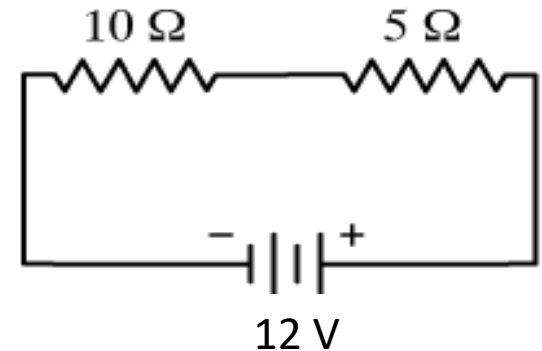- **Example 5 :**


In the circuit shown in the figure, two resistors R_1 and R_2 have been connected in parallel ?

Find: $R_{eq}, V_1, V_2, I_1, I_2, I_{eq}$



Preflight

Preflight

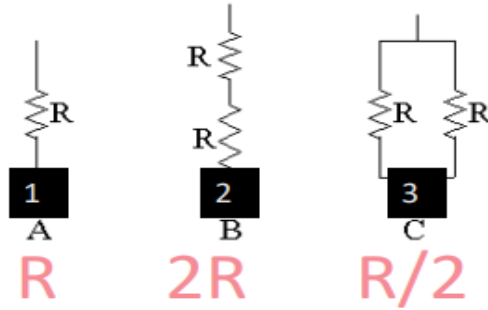

Which configuration has the **smallest** resistance?

- 1
- 2
- 3

Which configuration has the **largest** resistance?

- 2

summary

Electricity is like a water hose


Voltage

Volts (V)



Current

Amps (A or I)

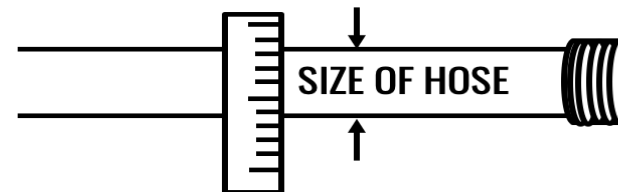

Resistance

Ohms (R or Ω)




FREEING
ENERGY

summary

•

Series Resistors

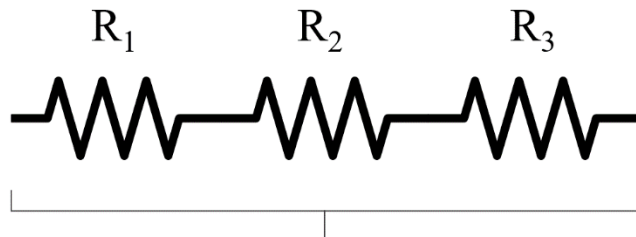
Current is the same across each resistor. Voltage is divided.



$$R_{Equivalent} = R_1 + R_2 + \dots + R_{N-1} + R_N$$

Parallel Resistors

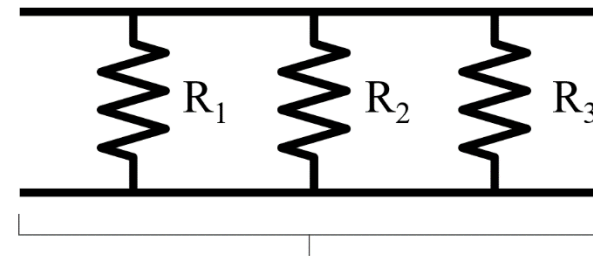Voltage is the same across each resistor. Current is divided.




$$R_{Equivalent} = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_{N-1}} + \frac{1}{R_N}}$$

summary

Series



Parallel

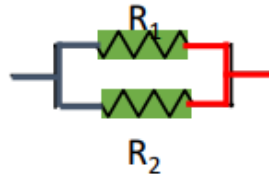

Wiring	Each resistor on the <u>same</u> wire.	Each resistor on a <u>different</u> wire.
Voltage	<u>Different</u> for each resistor. $V_{\text{total}} = V_1 + V_2$	<u>Same</u> for each resistor. $V_{\text{total}} = V_1 = V_2$
Current	<u>Same</u> for each resistor $I_{\text{total}} = I_1 = I_2$	<u>Different</u> for each resistor $I_{\text{total}} = I_1 + I_2$
Resistance	<u>Increases</u> $R_{\text{eq}} = R_1 + R_2$	<u>Decreases</u> $1/R_{\text{eq}} = 1/R_1 + 1/R_2$

Example 6

- Find **power** $P?$, if resistance $R= 50\Omega$

$V=220\text{ v}$?


Capacitors

- A **capacitor** is a two-terminal electrical device that can store energy in the form of an electric charge.
- Capacitors may be connected in **series** or in **parallel** to obtain a resultant value which may be either the sum of the individual values (in parallel) or a value less than that of the smallest capacitance (in series).


Series circuit



Parallel circuit

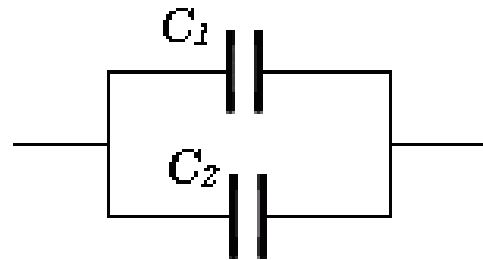

What is capacitor?

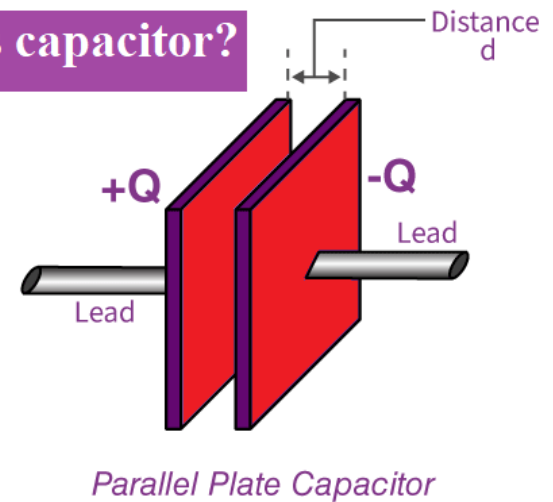

Capacitors

- How can we calculate the equivalent value in capacitors?

Series Capacitances


$$C_{\text{total}} = \frac{1}{\frac{1}{C_1} + \frac{1}{C_2} + \dots + \frac{1}{C_n}}$$

Parallel Capacitances

$$C_{\text{total}} = C_1 + C_2 + \dots + C_n$$

Capacitor in series

Capacitors in Series:

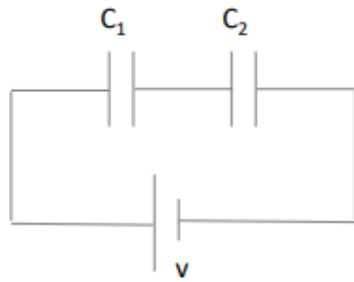


For capacitors in series the charge on the plates is the same.

$$C_{eq} = \left(\frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} \right)^{-1}$$

Capacitor in series

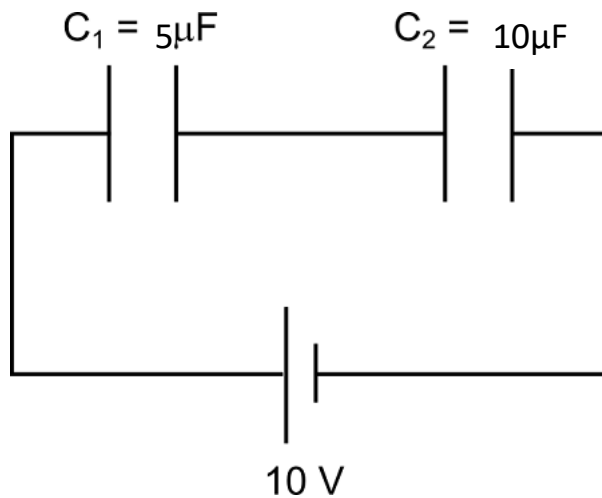
- Example 7:

- What is the total capacitance for the circuit presented below ?



Capacitor in parallel


Capacitors in Parallel:

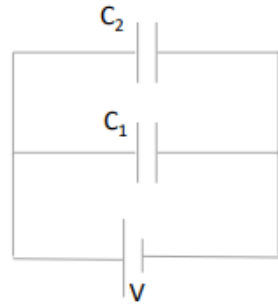

$$C_{\text{eq}} = C_1 + C_2.$$

Capacitor in parallel

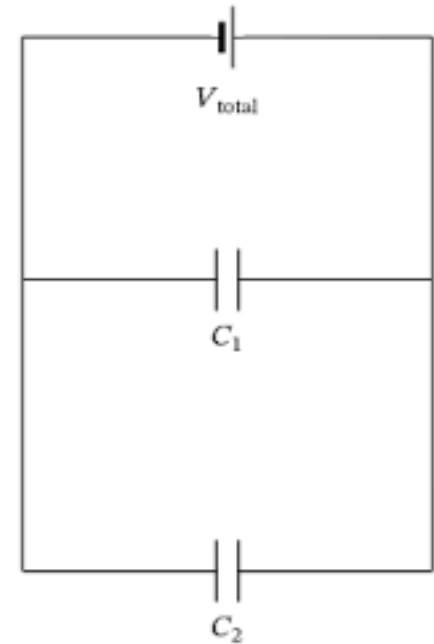- Example 8:
- What is the total capacitance for the circuit presented below ?
- if $C_1 = 20\mu F$, $C_2 = 50\mu F$




combination circuit

- A combination circuit is one that has a "combination" of series and parallel paths for the electricity to flow. Its properties are a combination of the two.

Example: Find the value of a single capacitor that replaces the three in the circuit below if

$$C_1 = C_2 = C_3 = 12 \mu\text{F}.$$

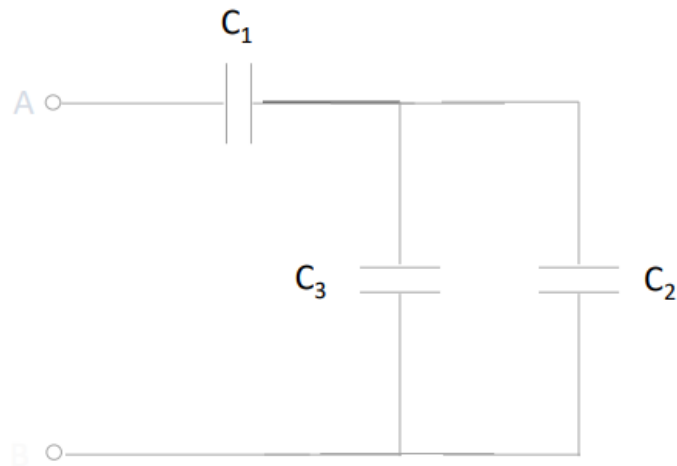

C_2 and C_3 are in parallel


$$C_{23} = C_2 + C_3$$

$$C_{23} = C_2 + C_3 \\ = 24 \mu\text{F}$$

combination circuit

Example continued:

The circuit can be redrawn:

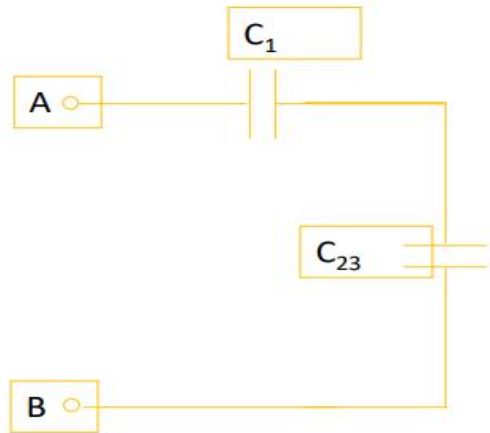

The remaining two capacitors are in series. $C_{eq} = \left(\frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} \right)^{-1}$




Is the final, equivalent circuit.

Question 1

Calculate the total resistance of the given circuit

ANSWER

$$R_{eq} = 450\Omega$$

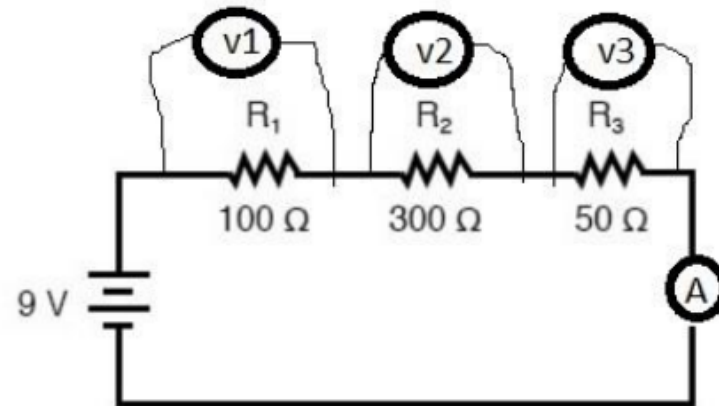


Question 2

Calculate the total current (I) generated by the battery in the circuit given below.

ANS

$$I = 0.02\text{A}$$

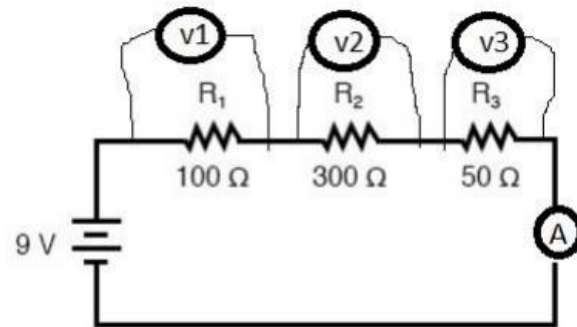

Question 3

Calculate **power dissipated (P)** in across an electric machine which draws **current R= 44 Ω** and connected to main supply **v = 220 V**.

Ans

$$P = V * I$$

$$\text{AND } I = V/R$$

1100 W.

Question 4

1.

In the circuit given below which of the resistors would draw maximum potential drop(V)?

2. Where you would connect the voltmeter to measure the total voltage?

